



EECS 151/251A

Spring 2024

Digital Design and Integrated Circuits

Instructor:

John Wawrzynek

Lecture 12: Timing part 2



Modeling Gate Delay

Inverter Transient Response


With:

resistive approximation for FETs,
high-to-low (HL)


$$V(t) = V_0 e^{-t/RC}$$

$$t_{1/2} = \ln(2) \times RC$$
 
$$t_{pHL} = f(R_{on} C_L) \\ = 0.69 R_n C_L$$




(a) Low-to-high

 



(b) High-to-low

The Switch – Dynamic Model (Simplified)

 


Transistor Sizing

  What happens if we make a MOSFET W times larger (wider)?




Switch Parasitic Model

The pull-down switch (NMOS)

 

Minimum-size switch

 


Sizing the transistor (factor W)

We assume transistors of minimal length (or at least constant length).


pFET Switch Parasitic Model

For traditional CMOS processes, pFETs are ~twice as resistive as nFETs.
(Mobility of holes is 1/2 that of electrons).


The pull-up switch (PMOS)

 

Minimum-size pFET

 

Sized for symmetry

 


General sizing

“Balanced” Inverter Parasitic Model

Drain and gate capacitance of transistor are **directly** related by process parameter ($\gamma \approx 1$)


$$C_D = \gamma C_G$$

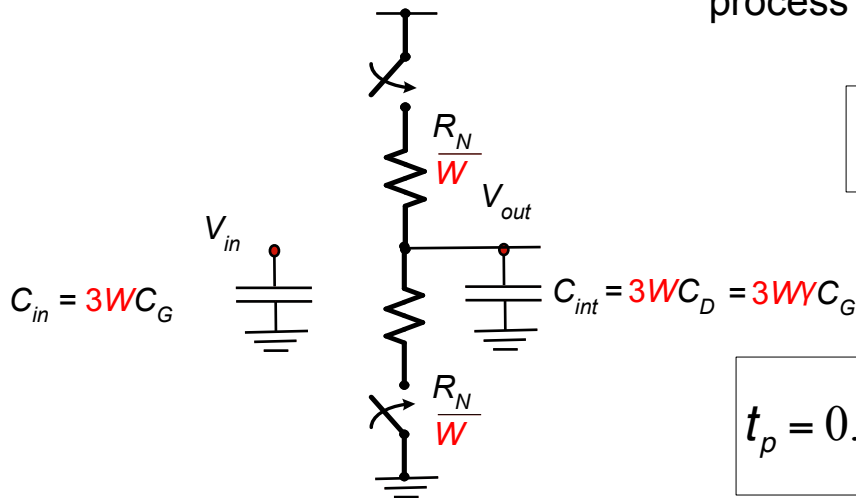

$$t_p = 0.69 \left(\frac{R_N}{W} \right) (3W\gamma C_G) = 0.69(3\gamma) R_N C_G$$

$= t_{p0}$ Intrinsic delay of inverter
independent of size

Inverter with Load Capacitance

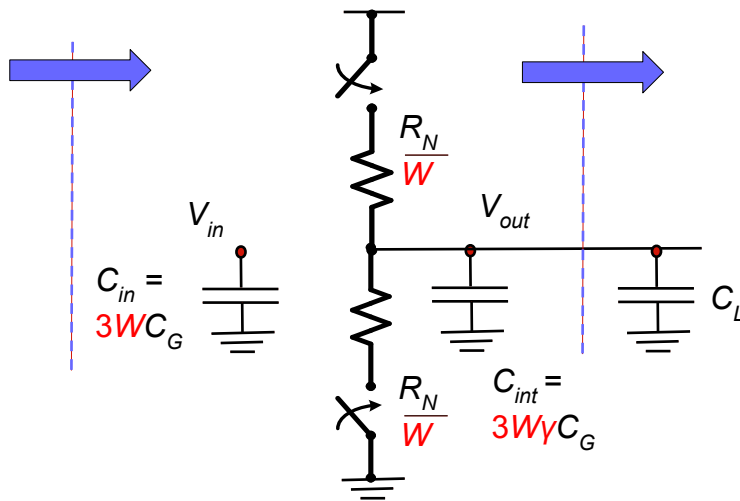

$$t_p = 0.69(R_N/W)(C_{int} + C_L)$$

$$= 0.69(R_N/W)(3W\gamma C_G + C_L)$$

factor out $3W\gamma C_G$

replace $C_{in} = 3WC_G$

$$= 0.69(3\gamma R_N C_G)(1 + \frac{C_L}{\gamma C_{in}})$$

$$= t_{p0}(1 + \frac{C_L}{\gamma C_{in}}) = t_{p0}(1 + f/\gamma)$$


f = **electrical fanout** = ratio of load capacitance (C_L) to and input capacitance (C_{in})

Inverter Delay Model

Delay linearly proportional to fanout, f .


For $f=0$, delay is intrinsic inverter delay $t_{inv} = t_{p0}$

$$t_p = t_{p0}(1 + f/\gamma)$$

 

Question: how does transistor sizing (W) impact delay?

Gate Delay Summary

 

The y-intercepts (intrinsic delay) for NAND and NOR are both twice that of the inverter. The NAND line has a gradient $4/3$ that of the inverter (steeper); for NOR it is $5/3$ (steepest).

$$t_{p0} \left(2 + \frac{4f}{3\gamma} \right)$$

2-input NAND

$$t_{p0} \left(2 + \frac{5f}{3\gamma} \right)$$

2-input NOR

What about gates with more than 2-inputs?


4-input NAND:

$$t_p = t_{p0} \left(4 + \frac{2f}{\gamma} \right)$$


intercept slope

Adding Wires to gate delay

 - ▶ Wires have finite resistance, so have distributed R and C :




 with r = res/length, c = cap/length, $\Delta t \propto r c L^2 \cong rc + 2rc + 3rc + \dots$



- ▶ Wire propagation delay is around half of what it would be if R and C were "lumped": $t_p = 0.38(rL * cL) = 0.38rcL^2$

Gate Driving long wire and other gates

 


$$R_w = r_w L, \quad C_w = c_w L$$


$$\begin{aligned} t_p &= 0.69R_{dr}C_{int} + 0.69R_{dr}C_w + 0.38R_wC_w + 0.69R_{dr}C_{fan} + 0.69R_wC_{fan} \\ &= 0.69R_{dr}(C_{int} + C_{fan}) + 0.69(R_{dr}c_w + r_wC_{fan})L + 0.38r_wc_wL^2 \end{aligned}$$

Driving Large Loads

 - ❑ Large fanout nets: clocks, resets, memory bit lines, off-chip
- ❑ Relatively small driver results in long rise time (and thus large gate delay)



- ❑ Strategy:

 


- ❑ How to design for optimal performance (least delay)?
- ❑ Should be obvious that total delay is minimized with **equal delay at each stage.**


Driving Large Loads

□ For some given C_L :

 - How many stages are needed to minimize delay?
- How to size the inverters?



 □ Get smallest delay if build one **very** big inverter




□ Not an interesting solution. Why?

- Something has to drive this inverter (a big inverter has a large input capacitance!) ...

Delay Optimization


□ First assume given:

 - A fixed number of inverters
- The size* of the first inverter
- The size of the load that needs to be driven



□ What is the minimal delay of the inverter chain?

 ** note: When we talk about inverter (or gate) “size”, we refer to the wide of the transistors making up the circuit.*



- Delay for the j -th inverter stage:

$$t_{p,j} = t_{p0} \left(1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right) = t_{p0} (1 + f_j / \gamma)$$

- Total delay of the chain:

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{j=1}^N \left(1 + \frac{C_{g,j+1}}{\gamma C_{g,j}} \right), \quad C_{g,N+1} = C_L$$

Optimum Delay


- ❑ Each inverter should be sized up by the same factor f with respect to the preceding inverter
- ❑ Therefore each stage has equal delay
- ❑ Given $C_{g,1}$ and C_L

$$f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$$

- ❑ Where F represents the overall fan-out of the circuit
- ❑ Therefore the minimal delay through the chain is:

$$t_p = N \cdot t_{p0}(1 + \sqrt[N]{F}/\gamma)$$

Example

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F} = \sqrt[3]{8} = 2$$

Delay Optimization

- Now assume given:
 - The size of the first inverter
 - The size of the load that needs to be driven
- Minimize delay by finding optimal number and sizes of inverters
- So, need to find N that minimizes:

$$t_p = N \cdot t_{p0}(1 + \sqrt[N]{F/\gamma}), \quad F = C_L/C_{g,1}$$

Finding optimal fanout per stage

$$t_p = N \cdot t_{p0}(1 + \sqrt[N]{F}/\gamma), \quad F = C_L/C_{g,1}$$

□ Differentiate w.r.t. N and set = 0:


$$\gamma + \sqrt[N]{F} - \frac{\sqrt[N]{F} \ln F}{N} = 0$$

$$\Rightarrow \boxed{f = e^{(1+\gamma/f)}} \quad f = \sqrt[N]{F}$$


□ Closed form only if : $\gamma = 0 \Rightarrow N = \ln(F), f = e$

Optimum Effective Fanout f

 - Optimum f for given process depends on γ





In Practice: Plot of Total Delay

 

- Why the shape?
- Curves very flat for $f > 2$
 - Simplest/most common choice: $f = 4$

Transistor Sizing in Logic Circuits

- ❑ Similar optimization challenges exist within all combinational logic blocks. How do we size transistors to minimize a given circuit?
- ❑ ASIC standard cell libraries include cells with various output drive strength (transistor sizes)
- ❑ Tools will automatically choose the proper size and/or add buffers to minimize critical path logic delay
- ❑ Hand methods exist for minimizing logic path delay:

  

End of lecture 12