

# EECS 151/251 A

## Discussion 8: Midterm Concept Review

March 8, 2024

Kevin Anderson (he/him)


# Overview

- GSIs have not seen the midterm so we know nothing! Do not ask us questions!
- This review was created to cover important topics
- Review composed of two parts


# Part 1: Circuitry

- Transistors (Layout)
- CMOS Static Circuits
- FPGA LUTs and Interconnect
- KMap

# Circuit Layouts

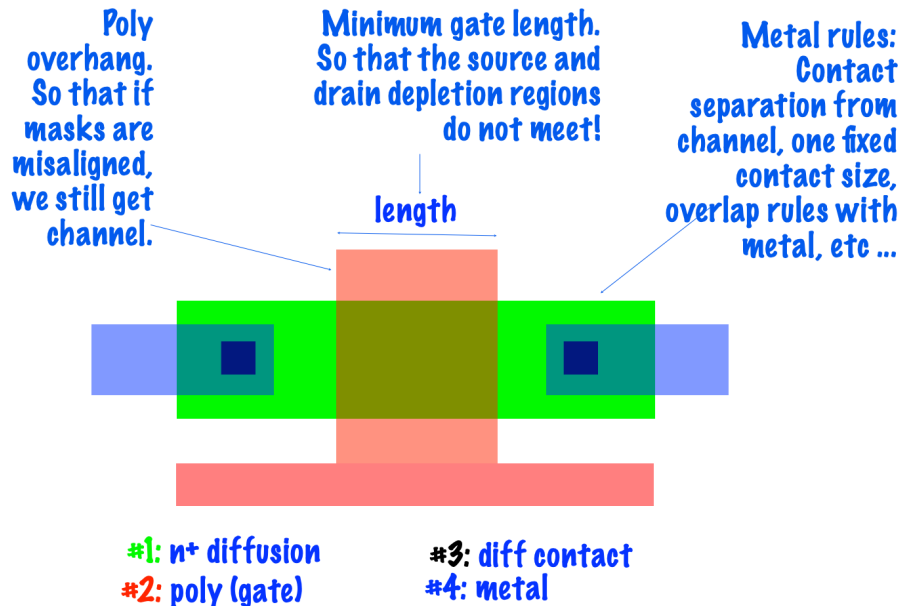

 - A layout is a top-down view of a transistor. It is another perspective of transistor
- Polysilicon represents the gate
- Boxes with or without X represents via




# Circuit Layouts

Steps:

1. Identify transistors
2. Separate PUN and PDN
3. Look at transistors connected to rails
4. Find shared diffusion regions and metal with via to discover inter-transistor connections

This is a AND gate

 


# Static CMOS Circuits

- PUN and PDN with single output
- Transistors in series represents a logical AND
- Transistor in parallel represents a logical OR
- PUN and PDN are duals; Boolean expression is the negation of the other
- Also simplify Boolean expression before drawing circuit

 
# Static CMOS Circuits

- Let's write the Boolean expression for this circuit:
- On your own, draw the circuit for an XNOR:


 
# Static CMOS Circuits




- What part of the static CMOS circuit is this?
- Draw the other half of the CMOS circuit




 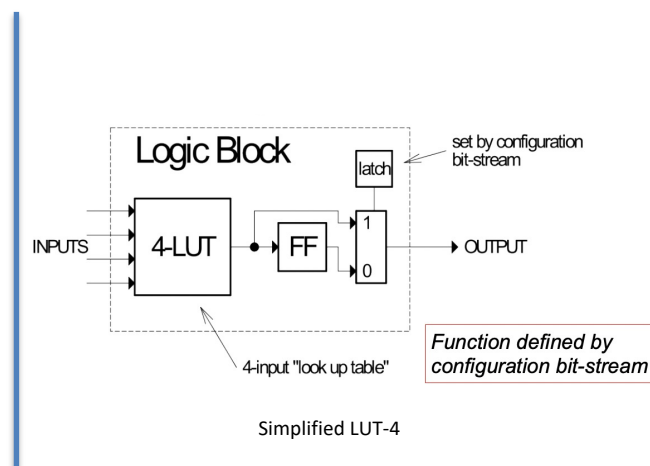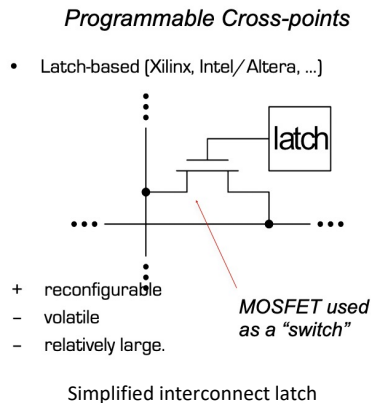
# FPGA

- FPGAs is a configurable HW platform (i.e. not fixed function)
  - The configurability comes from the interconnect and LUT
- Xilinx Logic Element Hierarchy: LUTs → Slice → CLBs
- Interconnect has latches to connect CLBs together
- There are no gates in an FPGA**
- How many logical expressions can a LUT-X hold?



Xilinx Series 7 CLB architecture

# Karnaugh Map

- Write the optimal SOP and POS:

	$\overline{cd}$	$\overline{c}d$	$cd$	$c\overline{d}$
$\overline{a}b$	1	0	1	0
$\overline{a}\overline{b}$	-	1	1	-
$ab$	0	1	0	0
$a\overline{b}$	0	-	-	-

# Karnaugh Map

- All KMaps must be Gray coded
- Write the optimal SOP and POS:

	$\overline{c}d$	$\overline{c}\overline{d}$	$cd$	$c\overline{d}$
$\overline{a}b$	1	0	1	0
$\overline{a}\overline{b}$	-	1	1	-
$ab$	0	1	0	0
$a\overline{b}$	0	-	-	-



	$\overline{c}d$	$\overline{c}\overline{d}$	$cd$	$c\overline{d}$
$\overline{a}b$	1	0	1	0
$\overline{a}\overline{b}$	-	1	1	-
$ab$	0	1	0	0
$a\overline{b}$	0	-	-	-

$$\text{SOP: } \overline{A}B + \overline{B}CD + A\overline{C}D + \overline{A}\overline{C}\overline{D}$$

# Karnaugh Map

- All KMaps must be Gray coded
- Write the optimal SOP and POS:

	$\overline{c}d$	$\overline{c}\overline{d}$	$cd$	$c\overline{d}$
$\overline{a}b$	1	0	1	0
$\overline{a}\overline{b}$	-	1	1	-
$ab$	0	1	0	0
$a\overline{b}$	0	-	-	-



	$\overline{c}d$	$\overline{c}\overline{d}$	$cd$	$c\overline{d}$
$\overline{a}b$	1	0	1	0
$\overline{a}\overline{b}$	-	1	1	-
$ab$	0	1	0	0
$a\overline{b}$	0	-	-	-

POS:  $(\overline{A} + \overline{B} + \overline{C})(\overline{C} + D)(B + C + \overline{D})(\overline{A} + C + D)$

# To-Know


- Boolean Algebra
- Cost Analysis (NRE and Recurring Cost)
- NMOS and PMOS
- CMOS Fabrication Process
- CMOS Circuits for Common Logic Gates (**NAND** and **INV**)
- FPGA vs ASIC
- PMOS weak pull down, NMOS weak pull up
- Timing diagram

# Part 2: Verilog and Blocks

- Positive-Edge FF
- Finite State Machines
- Verilog Basics
- Verilog Advanced

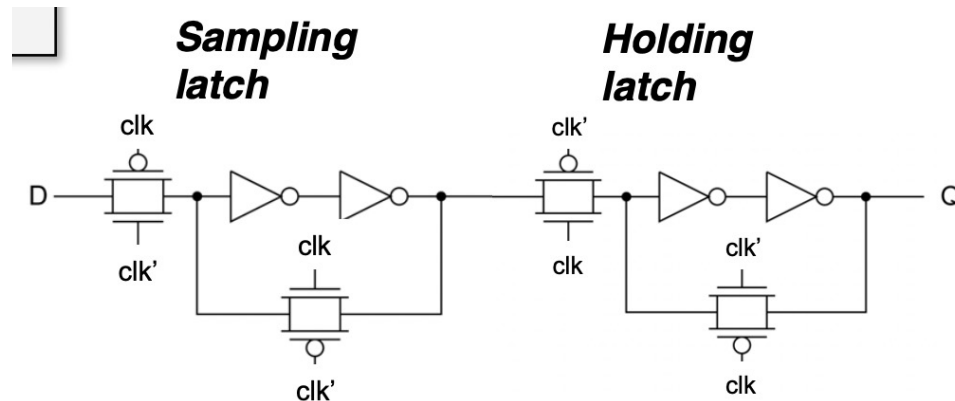
# Positive Edge Flip-Flop

- Flip-flop is composed of two latches
- Transmission gates orchestrate exchange between latches


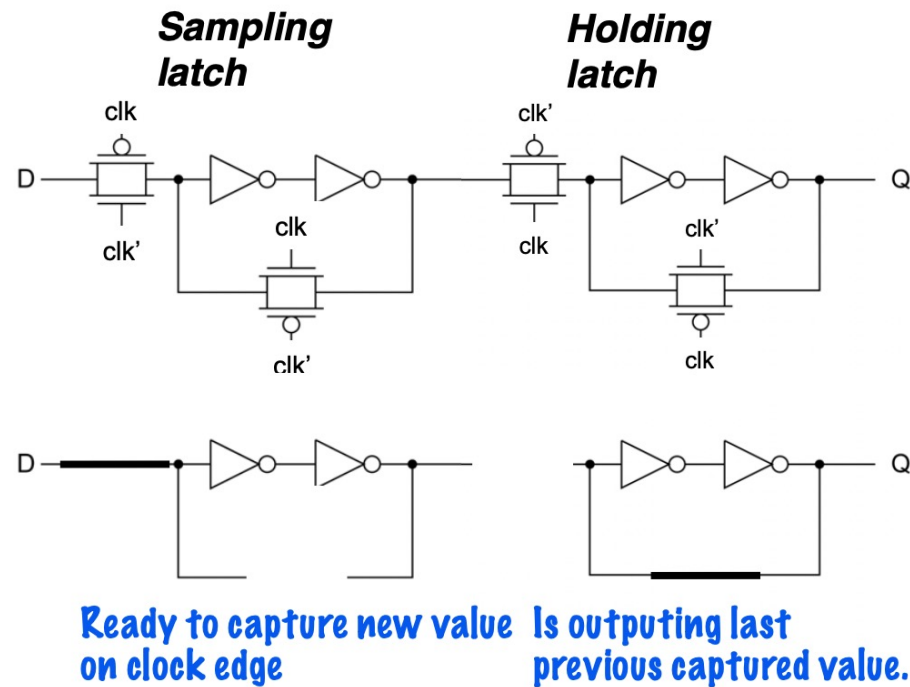
# Positive Edge Flip-Flop


- What is the clock state represented by the figure below?





 
# Finite State Machines

- Mealy vs Moore
- One-hot vs Binary vs BCD Encoding
  - BCD not really used for FSMs, but good to know the encoding
  - Gray Coding and Hamming Distance (for Binary and BCD only)
- State Diagrams
  - Idle state
  - Transitions without conditions taken on following cycle always. Transitions with condition taken on cycle when condition is met
  - Outputs that change on transition are Mealy. Outputs that change within state are Moore. If outputs change on both, then it's a mixture of both




Conceptual diagram of Mealy

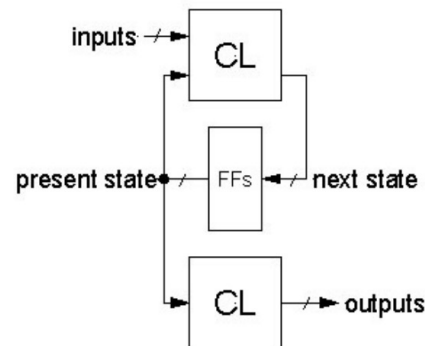

Conceptual diagram of Moore

# Finite State Machines

- Verilog FSM from discussion 5

 


State LSb

Truth Table

	A	B	C	D	Y
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0

SOP:  $\bar{A}D + \bar{A}B$

CD \ AB	00	01	11	10
00	0	1	0	0
01	1	1	0	0
11	1	1	0	0
10	0	1	0	0

 


State MSb

Truth Table

	A	B	C	D	Y
0	0	0	0	0	0
1	0	0	0	1	1
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	0
15	1	1	1	1	1


SOP:  $BC + \bar{A}B$

CD \ AB	00	01	11	10
00	0	1	0	0
01	0	1	0	0
11	0	1	1	0
10	0	1	1	0

 
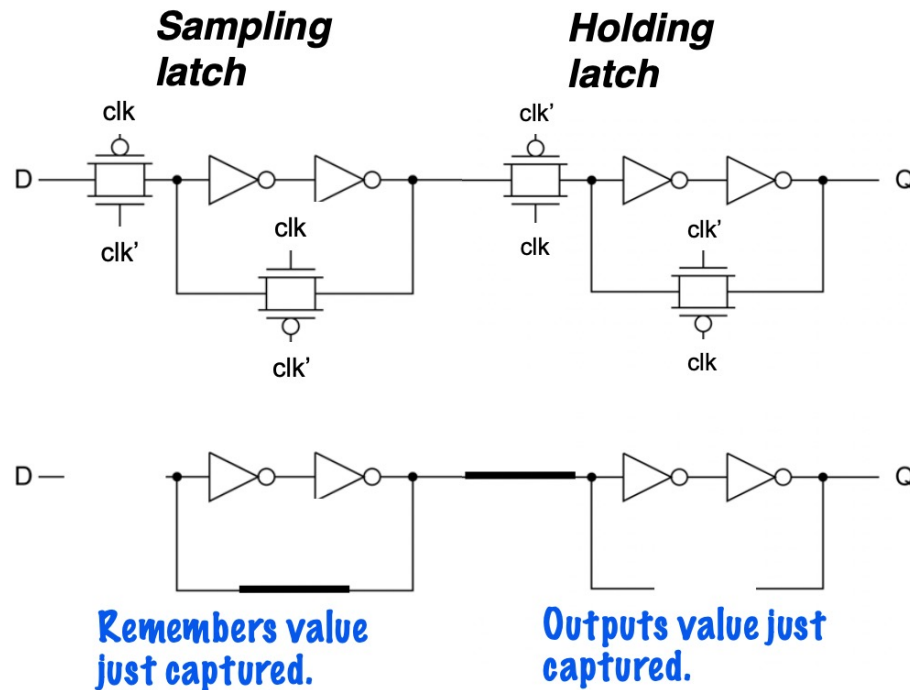
# Positive Edge Flip-Flop

- What is the clock state represented by the figure below?



# Verilog Basics

- **No register inference!**
- wire used in continuous assignment
- reg used in procedural assignment
- case statement for FSMs
- Use named ports for instantiation
- Width matters!!
  - e.x. `wire [1:0] tmp; assign tmp = 4;`

# Verilog Advanced

- FSMs must be written in style 2 (slide 37 Verilog Review) because no register inference
- Parameterized modules are generators
- generate creates copies of hardware that run in parallel
  - Types: generate for, generate if, generate case
  - Loops  $\neq$  generate

Example:

```
module naryand (in, out);
    parameter N = 1;

    input [N-1:0] in;
    output out;

    wire [N-1:0] tmp;
    buf(tmp[0], in[0]);
    buf(out, tmp[N-1]);
    genvar i;
    generate
        for(i = 1; i < N; i = i + 1) begin : ands
            and(tmp[i], in[i], tmp[i-1]);
        end
    endgenerate
endmodule

// Instantiation of generator
wire [4:0] f;
wire g;
naryand #(N(5)) and5(.in(f), .out(g));
```

# To-Know

- Transmission Gates
- Tri-state buffer vs Tri-state inverter
- Create state diagram from word problem
- Continuous Assignments and Procedural Assignments
- Ternary Operator
- Labelling state diagram
- Shift Register in Verilog